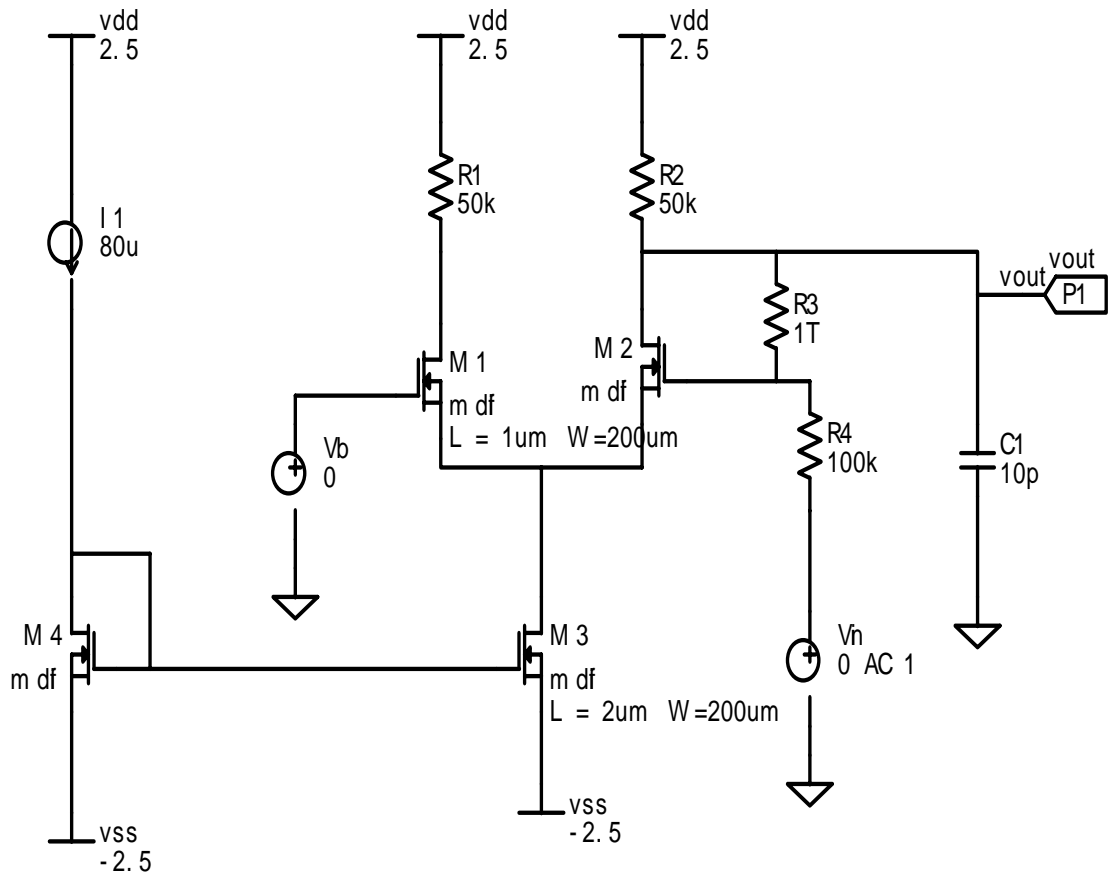


A differential pair amplifier with inverting feedback: reduce R3 from 1T to enable feedback effects. To improve the DC sweep, R1 can be made smaller than R2. It is easier to make this circuit work with larger supplies, such as 5v and -5v. Larger supplies would need adjustments of I1 and R1, R2. Also, the bias current of 80uA can be increased, but then also adjust R2 to keep The DC output bias near midrail.



$$I_b = 0.5 * \mu_{Cox} * (W/L) * V_{ov}^2$$

$$\mu_{Cox} = 100 \mu A/V^2 = 0.1 mA/V^2 \quad W/L = 100 \quad \text{when } I_b = 50 \mu A = 0.05 mA,$$

then $V_{ov} = 0.1v$.

$$g_m = 2 * I_b / V_{ov} = \sqrt{2 * I_b * \mu_{Cox} * W/L} \quad \text{under the above conditions, } g_m = 1 mA/V$$

Open loop gain is $V_o/V_{in} = A(s) = A_o / (1 + s/w_p)$ with $w_p = 1/(R_T * C_L)$

$$R_T = R_L \parallel r_{ds} \text{ and } A_o = g_m * R_T \quad r_{ds} = r_o = V_a / I_b$$

if $R_T = 50K$, then $A_o = g_m * R_T = 50$ if $V_a = 10v$., and $I_b = 50 \mu A$, then $r_{ds} = 200K$

if $C_L = 10pF$, then $R_T * C_L = 0.5 \mu sec$, and $w_p = 2 \text{ Megrad/sec}$, and $f_p = 318KHz$

With feedback, closed loop gain is $A_{cl}(s) = K * A(s) / (1 + A(s) * B)$,

Where $B = R_1 / (R_1 + R_F)$ note: in above schematic R_F is R_3 and R_1 is R_4

$K = -(1 - B)$ for inverting amp.

Substituting $A(s)$ into $A_{cl}(s)$, one can show that the closed loop gain is reduced and the closed loop pole is changed.

$$A_{cl}(s) = [K * A_o / (1 + A_o B)] / [1 + s/w_{pcl}] \quad \text{where } w_{pcl} = w_p * (1 + A_o B) - \text{closed loop pole}$$

If the loading effects of the feedback network are included at the output node, then

$$A_o = g_m' * R_T' \quad \text{and } w_p = 1/(R_T' * C_L)$$

where $g_m' = g_m - 1/R_F$ and $R_T' = R_L \parallel r_{ds} \parallel R_F$