

ECE 265 – LECTURE 13

Interface to switches and LEDs

Lecture Overview

2

- Interfacing to a switch
 - ▣ Debounce a switch
 - ▣ Connection to LEDs.

- REF: Chapters 1, 6, and 9 plus the 68HC11 reference manual.


Switch inputs

- In most embedded systems where you use a microcontroller you need to sense the outside world. A lot of this sensing is done by switches activated at specific pressures, temperatures, humidity, etc. or a push button switch momentary switch activated by the user.
 - ▣ Example: An automotive speed control. There is typically a switch on the brake (and clutch) pedal that disengages the speed control when it is pressed.
- Debouncing – The output of a switch at open and close is very, very noisy with multiple spikes in voltage. If not correctly debounced, these spikes could be seen as multiple switch closures (openings).

Debounce

4

- A de-bounce circuit
- In a typical application the switch signal is input to the microcontroller pin. Inputs to the chip need to be connected such that they are always driven to either Vdd or GND.
- The resistor is needed to current limit the circuit when the switch is closed and the output is a logic 0.
 - ▣ In a system with VDD of $\sim 5V$ and a limit resistor of 330 ohms this gives a current of 0.015 Amp

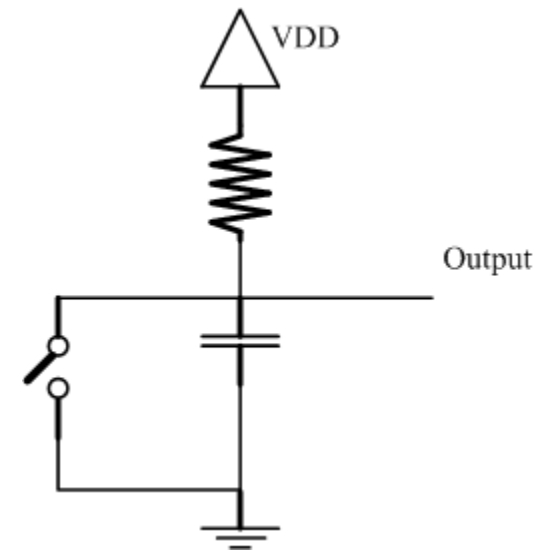

A note on connection to pins

5


- All input pins on the chip **MUST** be connected to an input signal, or connected to Vdd or GND as appropriate.
- No input pin can be left floating. Why?

Switch DIP packages

6

- For computer interface there are DIP package switches.

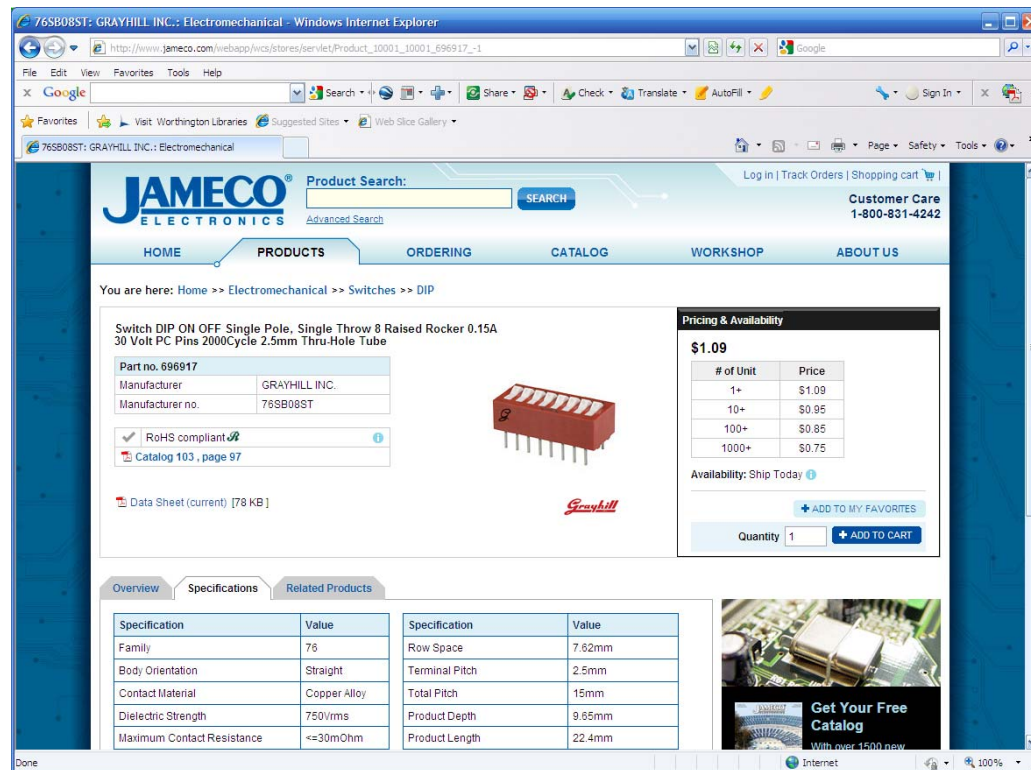For these the interface is the same as the switch interface looked at before.



The screenshot shows a web browser window displaying the Jameco Electronics website. The page is for a product titled "Switch DIP ON OFF Single Pole, Single Throw & Raised Rocker 0.15A 30 Volt PC Pins 2000Cycle 2.5mm Thru-Hole Tube". The product is shown as a red DIP switch component. The page includes a navigation menu, a search bar, and a pricing table. The pricing table shows the following information:

# of Unit	Price
1+	\$1.09
10+	\$0.95
100+	\$0.85
1000+	\$0.75

Below the pricing table, there are buttons for "ADD TO MY FAVORITES" and "ADD TO CART". The page also includes a "Specifications" section with two tables:


Specification	Value
Family	76
Body Orientation	Straight
Contact Material	Copper Alloy
Dielectric Strength	750Vrms
Maximum Contact Resistance	<=30mOhm

Specification	Value
Row Space	7.62mm
Terminal Pitch	2.5mm
Total Pitch	15mm
Product Depth	9.65mm
Product Length	22.4mm

Output to a LED device

7

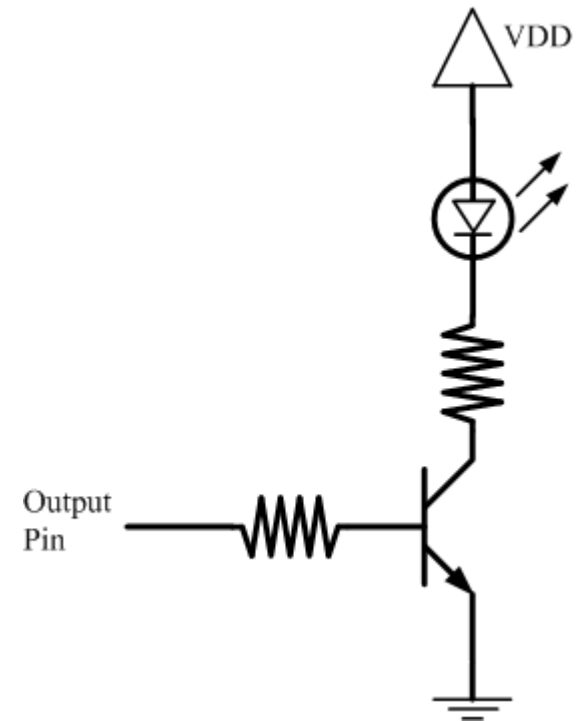
- LEDs are often used as output devices.
- Single LED as a status indication.
- 7-Segment displays –
 - ▣ Each segment of display is a LED
- A positive logic circuit for driving a LED
- driving a LED
 - ▣ Output is 0 – LED off
 - ▣ Output is 1 – LED on




LED and other devices

8

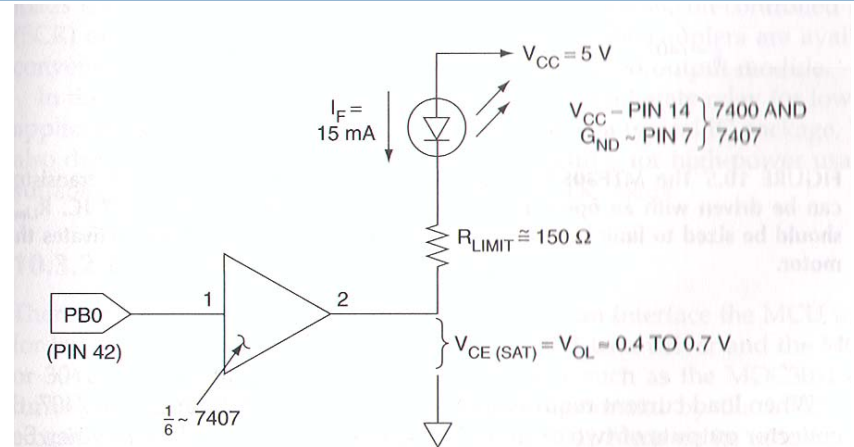- Interface to LED (0=on)
- Below
 - ▣ Interface to relay



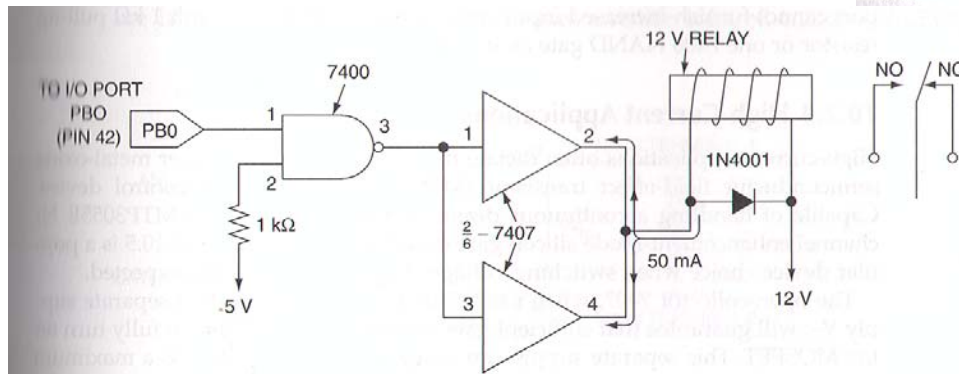(a) THE LED IS ON WITH A LOGIC 0 OR LOW INPUT AND OFF FOR A LOGIC 1 OR HIGH INPUT




(b) OPEN-COLLECTOR 7407 OUTPUTS ARE CONNECTED TOGETHER (WIRE-OR) TO DOUBLE CONTROL CURRENT CAPACITY. A LOW INPUT AT PBO OPERATES THE RELAY.

FIGURE 10.4 A single gate controls an LED in (a), and two wire-OR gates control a relay in (b).

LED interface

9

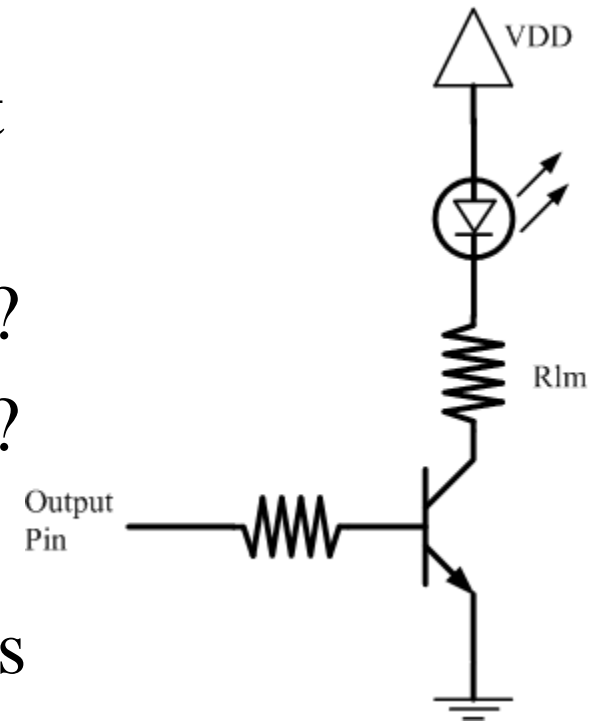
- Interface structure when interfacing to a switch or LED.
- This circuit is one possible output structure to do the interface.
- What happens when a 1 is output?
- What happens when a 0 is output?
- What is the value of R_{lm} ? Why is it needed?



The current limit resistors

10

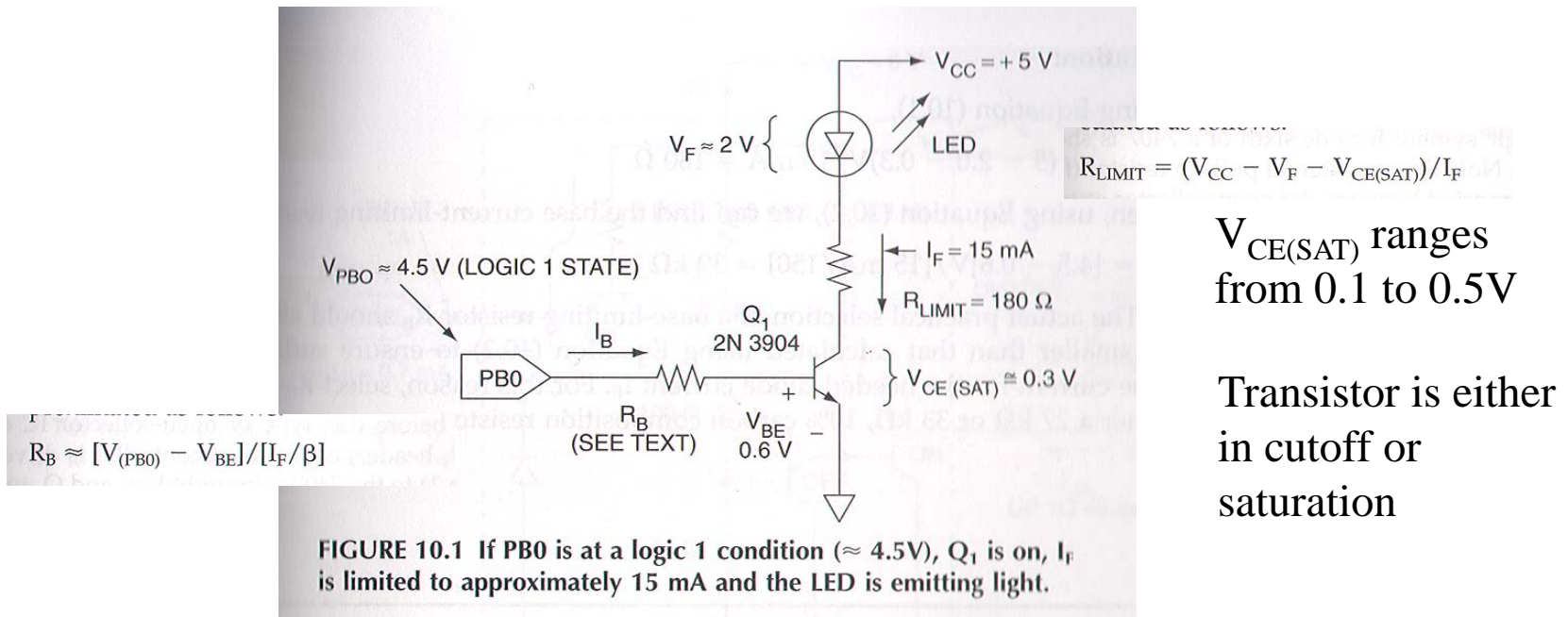- Example from the text shows how to size the resistors.



More on Resistor Sizing

Example 10.1:

The LED illustrated in Figure 10.1 is to be interfaced to port B using a 2N3904 small-signal general-purpose NPN transistor with a $V_{CE(SAT)}$ of 0.3 V and a typical value of beta (β) of 150. Assume $V_{(PB0)}$ is typically 4.5 V. Calculate both R_{LIMIT} and R_B .

Solution:

Using Equation (10.1),

$$R_{LIMIT} = (5 - 2.0 - 0.3)V/15 \text{ mA} = 180 \Omega$$

Then, using Equation (10.2), we can find the base current-limiting resistor,

$$R_B = [4.5 - 0.6]V/[15 \text{ mA}/150] = 39 \text{ k}\Omega$$

The actual practical selection of a base-limiting resistor R_B should always be smaller than that calculated using Equation (10.2) to ensure sufficient base current for the needed diode current I_F . For this reason, select R_B to be either a 27 k Ω or 33 k Ω , 10% carbon composition resistor.

Summary

12

- How do you interface a switch to the 68HC11
- How do you interface a LED or other device to the 69HC11.