



# Sequential Design Basics

---



# Lecture 2 topics

---

- A review of devices that hold state
  - A review of Latches
  - A review of Flip-Flops
  
- Unit 11 of text
  - Set-Reset Latch/Flip-Flops/D latch/  
Edge triggered D Flip-Flop



# Latches and Flip-Flops

---

- What is the difference?
  - Flip-flops use a clock and are clock edge triggered
    - When the clock edge occurs the data on the data inputs determines the next state of the flip-flop
  - Latches are level sensitive
    - Use a clock, and when the clock (or enable) is active the output of the latch follows the data input.
    - Latches are very common in VLSI circuits. (Used as they require fewer transistors.)



# The basis

---

- ❑ **How do you design logic that holds state?**
- ❑ Individual logic gates are feed forward devices who's output depends on the value of the inputs to that device.
- ❑ So how to create a device that holds a state?



# The basis



---

- **How do you design logic that holds state?**
- Individual logic gates are feed forward devices who's output depends on the value of the inputs to that device.
- So how to create a device that holds a state?
  - **FEEDBACK!!!**

# The Set-Reset (SR) Latch

- The circuit has no memory
  - Output depends not only on present inputs and the state of the latch when the current inputs were applied.
- The state 1 1 on the inputs is not allowed. Why?

FIGURE 11-5  
S-R Latch

  




# HDL code for SR Latch

---

- The core of the model
  - --set up dataflow for SR latch
  - $Q \leq R \text{ NOR } Q_{\text{bar}}$  AFTER 5 ns;
  - $Q_{\text{bar}} \leq S \text{ NOR } Q$  AFTER 5 ns;
- Apply stimulus to S and R
  - What does simulation show

# HDL simulation of SR latch

 



# The next state

- The state 11 is not allowed
- $S=1$   $Q$  to 1
- $R=1$   $Q$  to 0
- $S$  and  $R$  00
  - Hold state

		$S$	
		0	1
$RQ$	00	0	1
	01	1	1
	11	0	X
	10	0	X
	11	0	X

(a)  $Q^+$  map

$S$	$R$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

(b) Truth table

} Inputs not allowed

# Next state truth table

---

- From the table you can get the next state equation
  - Here –  $Q^+ = S + R'Q$
- An equation that expresses the state of a latch (or flip flop) in terms of its present state and inputs is referred to as the *characteristic equation*.

# The D Latch

- The D Latch is the most common element in CMOS design.

 


Figure 7-12 D latch: (a) circuit design using NAND gates; (b) function table; (c) logic symbol.


 


Figure 7-13 Functional behavior of a D latch for various inputs.


# Timing diagram for a D Latch

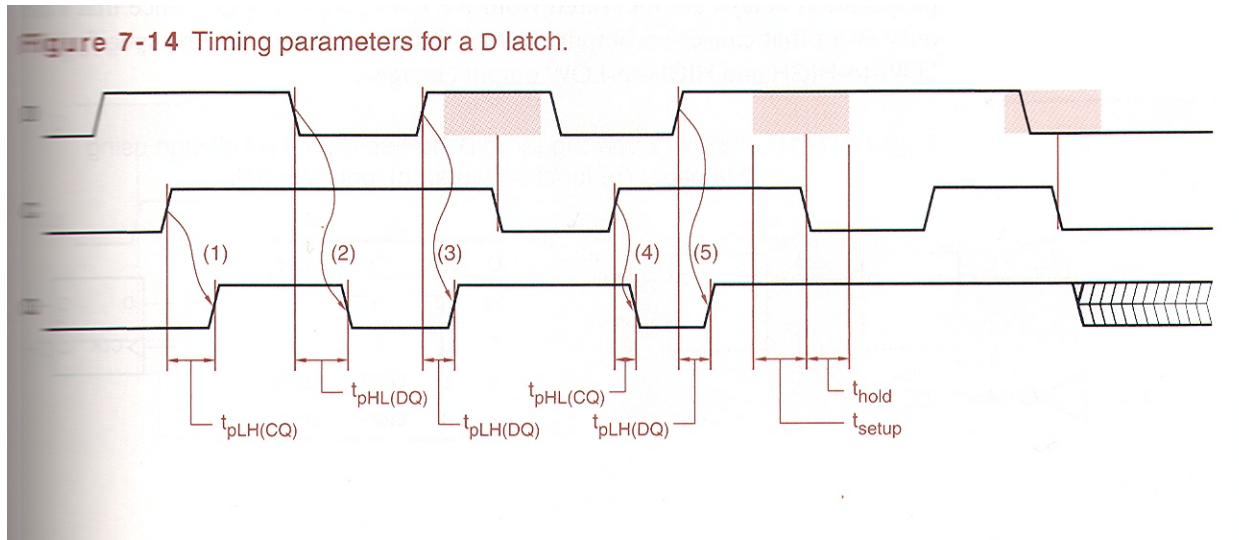

# The D F/F


- The D Flip-Flop has edge triggered operation
- Can be positive edge triggered (as here) or negative edge triggered

Figure 7-15 Positive-edge-triggered D flip-flop: (a) circuit design using D latches; (b) function table; (c) logic symbol.

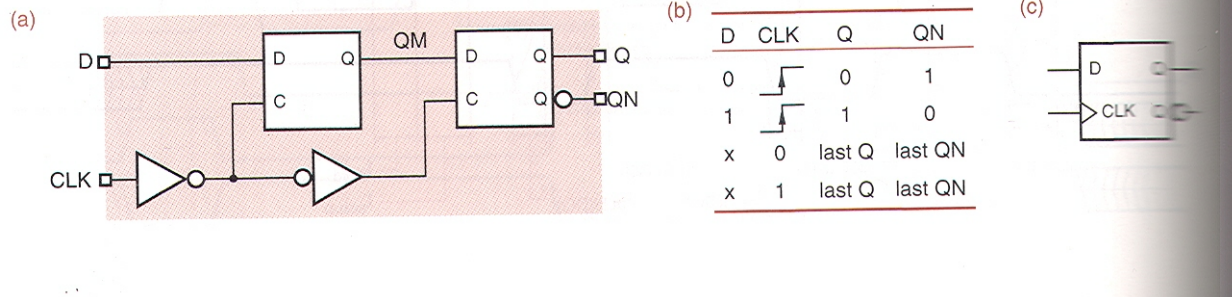


# Timing for a D Flip-Flop

- Important to note relationships

 

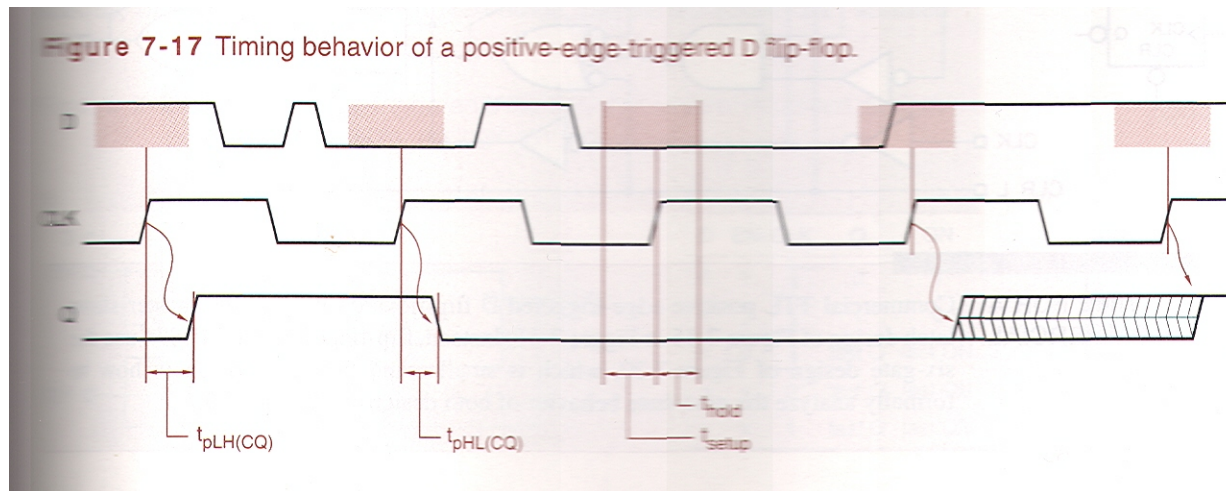
# D F/F Behavior

- Some important timing parameters
  - Clock to output
  - Setup and hold time


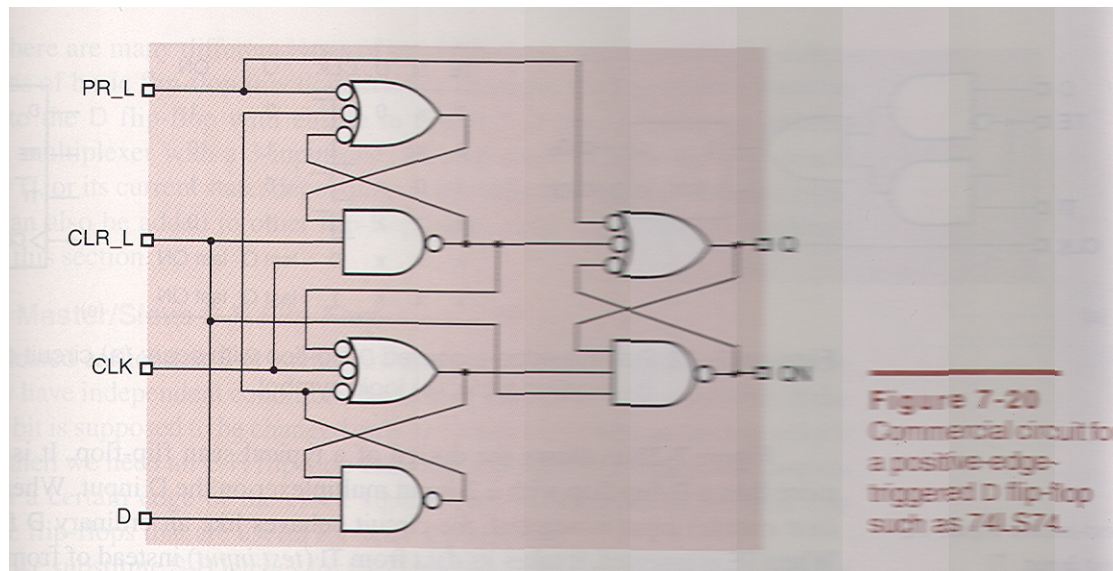
# D F/F with Preset and Clear


- Can add preset and clear for easier circuit initialization.





# Scan Chains


- D F/F is the F/F used in scan chains.

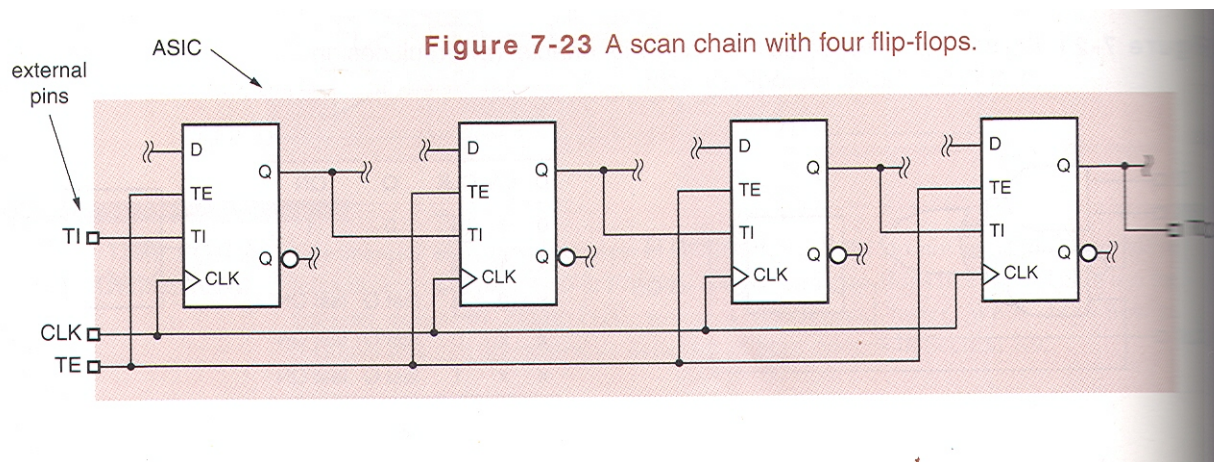

- What are scan chains?

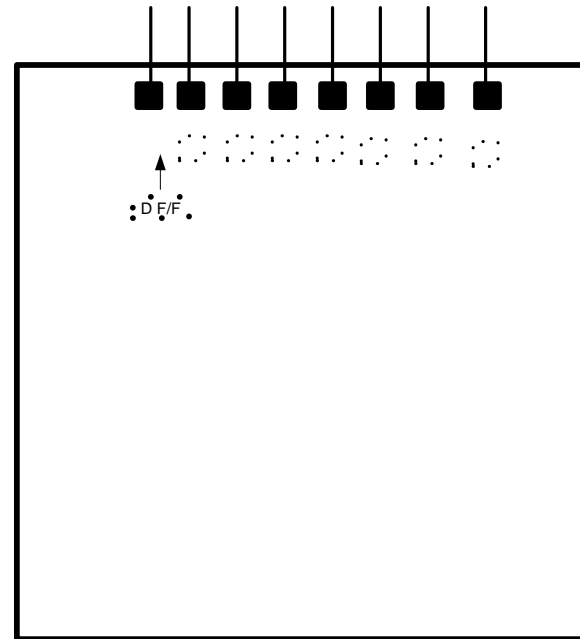
# Scan Chains

- Can use scan chains to inputs data or extract data



# The T Flip Flop


## □ Toggle Flip Flop

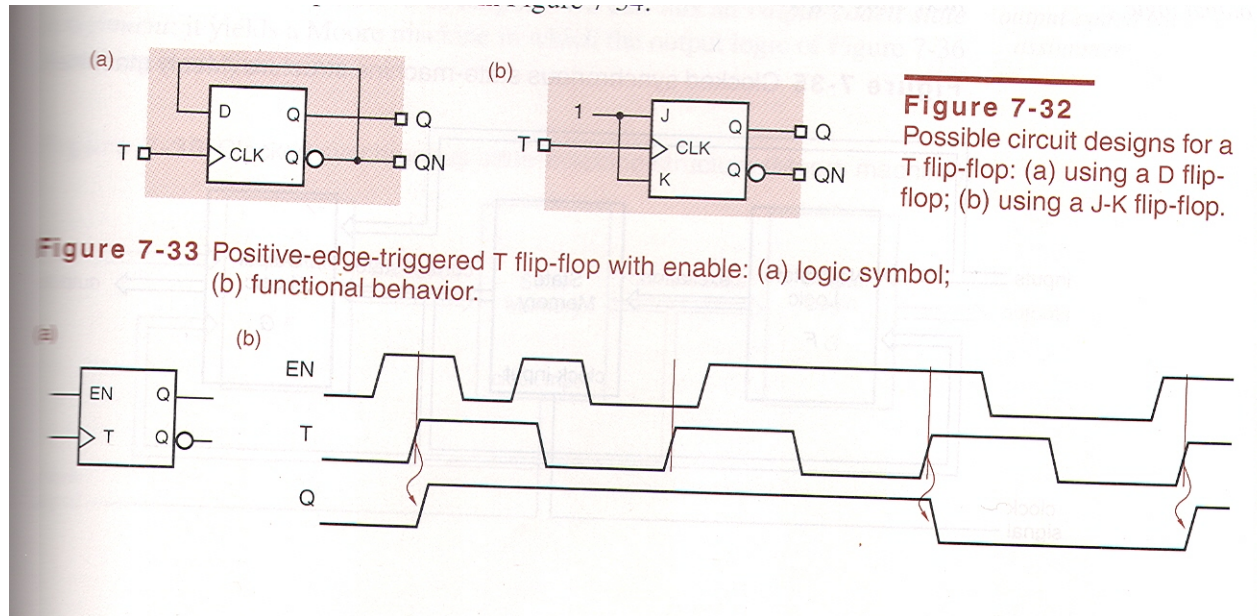

# More on Basic Sequential Elements

## □ The S-R F/F


- $Q^* = S + R'Q$

 

S	R	CLK	Q
0	0	↓	Q
0	1	↓	0
1	0	↓	1
1	1	↓	Not allowed

## □ The Toggle F/F

- $Q^* = Q'$

 


T	CLK	Q
0	↑	Q
1	↑	$\overline{Q}$

- $Q^*$  is next value or next state

# D F/F and J/K F/F

## □ D F/F


■  $Q^* = D$

 

D	CLK	Q
0	↑	0
1	↑	1

## □ J/K F/F


■  $Q^* = JQ' + K'Q$

 

J	K	CLK	Q
0	0	↑	Q
0	1	↑	0
1	0	↑	1
1	1	↑	$\overline{Q}$
 
# A simple up down counter


- Start with state diagram
- Control is  $x$



# Then add state table

□ Will use T F/Fs

table reflect T F/Fs

 

Pr St		Next State				T F/F inputs			
		x=0		x=1		x=0		x=1	
y1	y2	y1	y2	y1	y2	T1	T2	T1	T2
0	0	0	1	1	1	0	1	1	1
0	1	1	0	0	0	1	1	0	1
1	0	1	1	0	1	0	1	1	1
1	1	0	0	1	0	1	1	0	1

# K Maps for the toggle F/Fs

T1

		y1 y2		<u>y1</u>	
		00	01	11	10
x	0	0	1	1	0
	1	1	0	0	1

y2

T2


		y1 y2		<u>y1</u>	
		00	01	11	10
x	0	1	1	1	1
	1	1	1	1	1

y2

$$\begin{aligned} T1 &= x'y2 + x y2' \\ &= x \text{ xor } y2 \end{aligned}$$



# Implementation

 


# Some final notes

- Sequential elements (F/Fs) are bistable
- *Def:* Bistable – can be in one of two states


**Figure 7-2**

A pair of inverters forming a bistable element.

 

**Figure 7-3**

 
Transfer functions for inverters in a bistable feedback loop.



Transfer function:

$$V_{out1} = T(V_{in1})$$

$$V_{out2} = T(V_{in2})$$

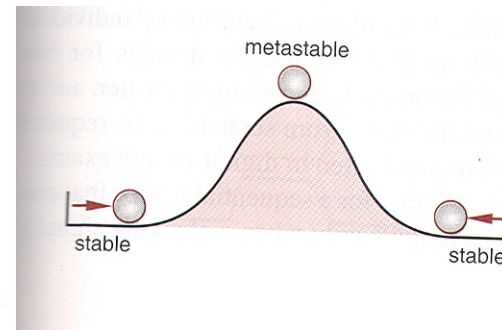

**Figure 7-4**

Ball and hill analogy for metastable behavior.




# Digital Circuit Types

---

- Combinational Logic Circuit – one whose outputs depend only on its current inputs.
  - A more descriptive term might be feedforward combinational logic circuits. These are circuits in which there is no feedback.
- Sequential Logic Circuit – one whose output depends not only on its current inputs, but also on the past sequence of inputs.
 
# State changes

- A sequential circuit changes its state at times specified by a clock
- Clock frequency  $C_f = 1 / T$ 
  - Where T is the Clock period





# Homework L2

---

- Read Unit 11
- Problem 11.1 – not for turn in – work for understanding – answer is in the text.
- (borrow a text or go to library)
- Go through the study guide of Unit 11