



# Common Elements in Sequential Design

---



# Lecture 3 topics


---

- Registers and Register Transfer
- Shift Registers
- Counters
  - Basic Counter
  - Partial sequence counters
  - Other counters
- State Machine Basics
  
- Review of solution to 11.1
- Units 11 and 14

# 11.1 solution from text


## □ The Problem

- | Assume that the inverter in the given circuit has a propagation delay of 5 ns and the AND gate has a propagation delay of 10 ns. Draw a timing diagram for the circuit showing  $X$ ,  $Y$ , and  $Z$ . Assume that  $X$  is initially 0,  $Y$  is initially 1, after 10 ns  $X$  becomes 1 for 80 ns, and then  $X$  is 0 again.

 

11.1

## □ The solution

 





# Register and Register Transfer

---

- Computers, embedded systems, and other digital devices usually have a data word of a given size.
- Where is the data when it is actively being used?
- Data is typically in a register => register is the size of the data
- Registers are implemented by D F/Fs grouped together.

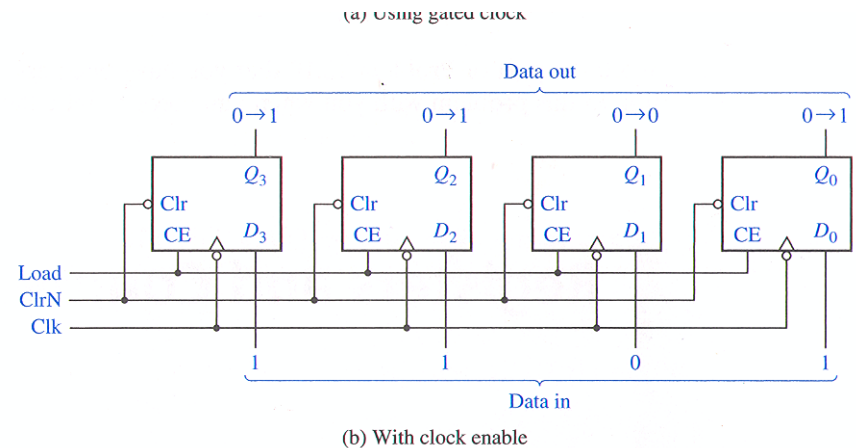
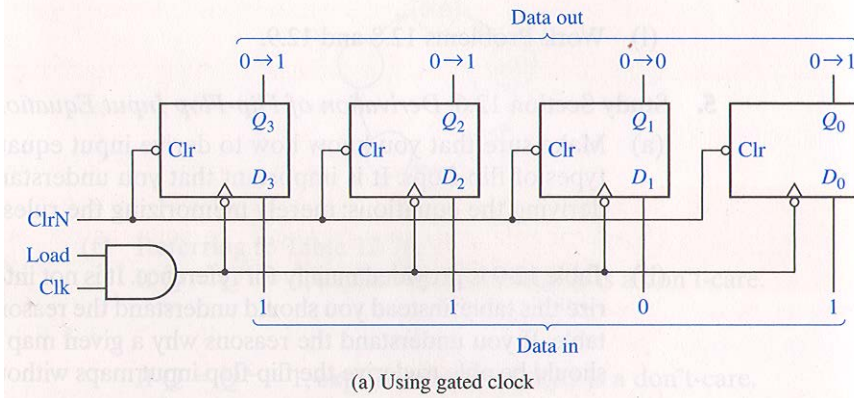
# Loading and using registers

- May have a gated clock or a setup with enable.
- May just have a load signal.


 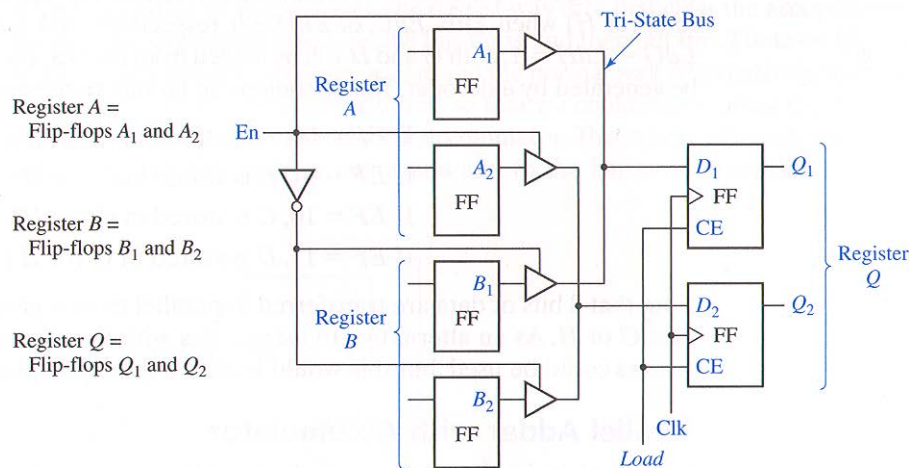
# When data needs to be moved


- Typically data is transferred between registers on tri-state busses.



# Register with tri-state output


## □ Logic Diagram

**FIGURE 12-3**  
Logic Diagram for  
8-Bit Register with  
Tri-State Output

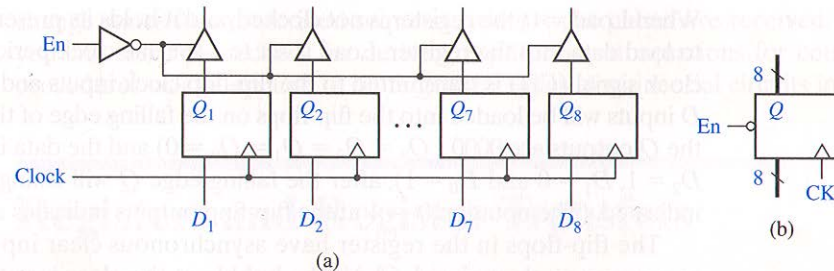

## Data transfer



**FIGURE 12-4**  
Data Transfer Using  
a Tri-State Bus

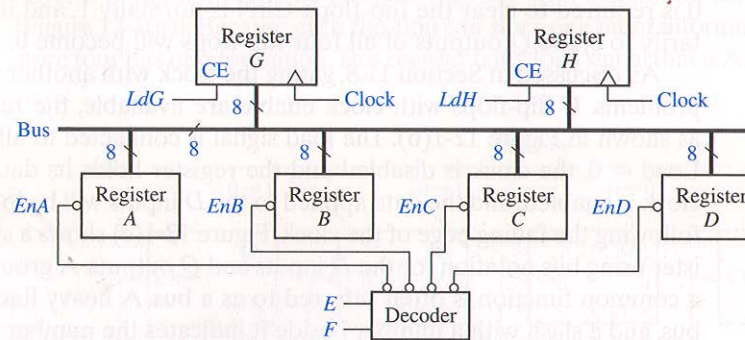

# Shift Registers

- Data can be shifted right, left, and sometimes both ways.

FIGURE 12-7  
Right-Shift Register

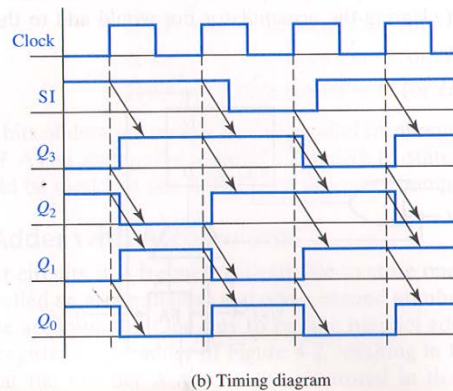 




# Binary Counters

## □ Simply count

FIGURE 12-13  
Synchronous  
Binary Counter

 


Present State			Next State			Flip-Flop Inputs		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

	C	0	1
BA	00	0	0
	01	0	0
	11	1	1
	10	0	0
		T <sub>C</sub>	

	C	0	1
BA	00	0	0
	01	1	1
	11	1	1
	10	0	0
		T <sub>B</sub>	

# Counter with D F/F

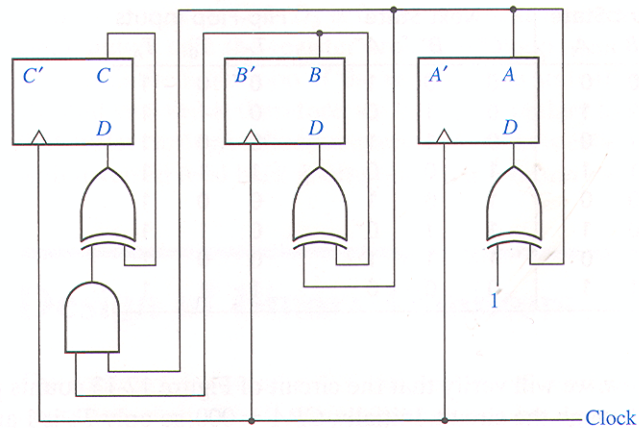

BA	0	1
00	0	1
01	0	1
11	1	0
10	0	1

$D_C$


BA	0	1
00	0	0
01	1	1
11	0	0
10	1	1

$D_B$


BA	0	1
00	1	1
01	0	0
11	0	0
10	1	1

$D_A$


□ Fig 12-15 and Fig 12-16

 

# Up/Down Counter

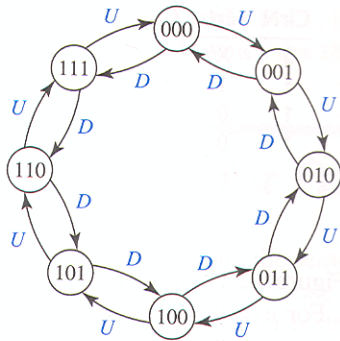

CBA	$C^+B^+A^+$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

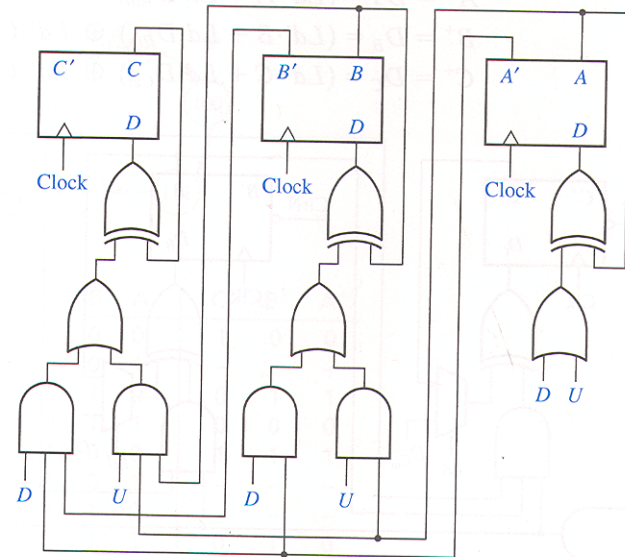




# Other sequences

---

- In a computer assignment you will implement a Gray Code counter. You should familiarize yourself with Gray Code. (wikipedia)
- From it you can see how to implement any counting sequence.
- Will not be covering counters with J-K F/Fs.
 
# State Machine Types

- In digital designs there are two fundamental ways that state machines are implemented
- Mealy Machine
  - Outputs are a function of the current state and the inputs




Mealy Machine

# State Machine Types (2)
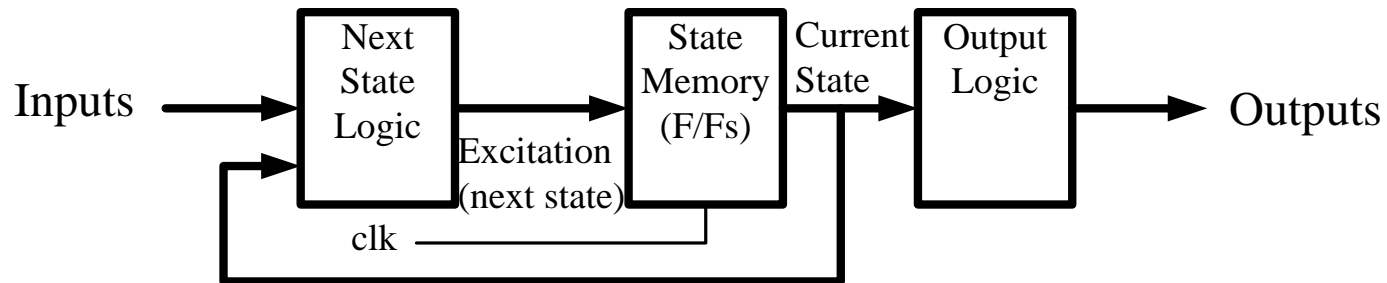
## □ Moore Machine

- Outputs are a function of the current state only



Moore Machine



# Some historical info

---

- Mealy machine is named after George H. Mealy who presented a paper in 1955, “A Method for Synthesizing Sequential Circuits.”
- Formal definition – A Mealy machine is a 6-tuple,
  - A finite set of states
  - A start state (initial state)
  - A finite set called the input alphabet
  - A finite set called the output alphabet
  - A transition function ( $T: S \times \Sigma \rightarrow S$ ) mapping pairs of a state and an input symbol to the corresponding next state.
  - An output function ( $G: S \times \Sigma \rightarrow \Delta$ ) mapping pairs of a state and an input symbol to a corresponding output symbol.



# Formal Definition of Moore Machine

---

- Moore machine is named after Edward F. Moore who presented a paper in 1956, “Gedanken-experiments on Sequential Machines.” (formulated)
- Formal Definition:
  - A finite set of states
  - A start state (initial state)
  - A finite set called the input alphabet
  - A finite set called the output alphabet
  - A transition function ( $T: S \times \Sigma \rightarrow S$ ) mapping a state and the input alphabet to the next state.
  - An output function ( $G: S \rightarrow \Delta$ ) mapping each state to the output alphabet.



# State Machine Design Process

---

- Either Traditional or Modern
- Tradition Design Methodology for creation of a state machine:
  - From a detail word specification of the problem generate a state graph or state table translating the word specification into a more formal description of the state machine.
  - If a state diagram is used, generate a state table
  - Pick the sequential element for implementation : D F/F, T T/F, J-K F/F, RS F/F
  - Select state machine type – Mealy or Moore
  - Generate the next state and output logic.



# State Machine HDL Design Process

---

- HDL Design Methodology for creation of a state machine:
  - From a detail word specification of the problem generate a state graph or state table translating the word specification into a more formal description of the state machine. Typically it will be a state graph.
  - Select state machine type – Mealy or Moore
  - Write the 3 processes of a HDL description that capture the specification.
    - The process that specifies the F/Fs
    - The process for generation of the next state
    - The process for generation of the outputs.



# Assignment

---

- Read and study textbook problems of Unit 11 and Unit 14.