



# L10 – State Machine Design Topics

---



# States Machine Design

---

- Other topics on state machine design
  - Equivalent sequential machines
  - Incompletely specified machines
  - One Hot State Machines
  
- Ref: text Unit 15.4, 15.5, 15.8



# Equivalent State Machines

---

- So far have seen that equivalent states in the state table of a sequential machine are equivalent and can be removed.
- How about the equivalence between two sequential circuits?
  - *Two sequential circuits are equivalent if they are capable of doing the same work.*


# Formally

---

- Definition 15.2
  - Sequential circuit  $N_1$  is equivalent to sequential circuit  $N_2$  if for each state  $p$  in  $N_1$ , there is a state  $q$  in  $N_2$  such that  $p \equiv q$ , and conversely, for each state  $s$  in  $N_2$  there is a state  $t$  in  $N_1$  such that  $s \equiv t$ .
  - Simply said they have the same states which can be seen if the circuit is small enough.
- An implication table can be used to prove this.
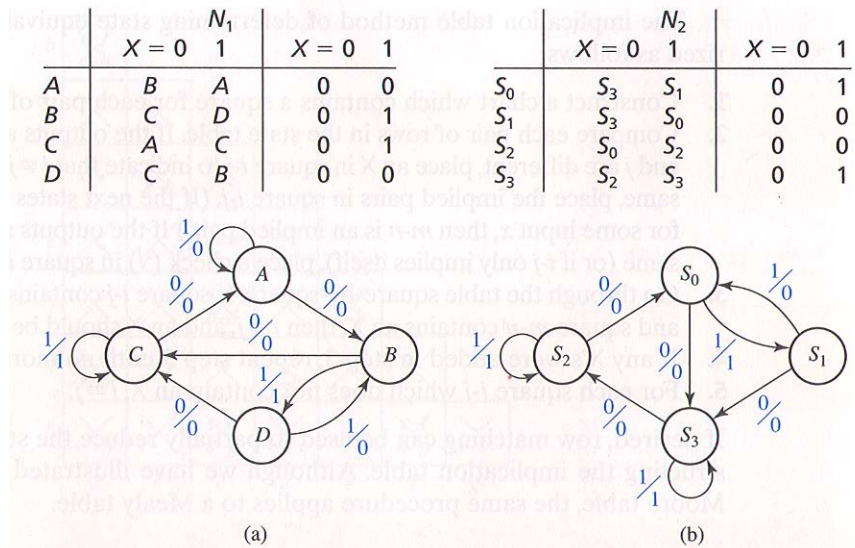
# An example

- State tables and state graphs of two sequential machines. Figure 15-6 from the text.
- Equivalent?






# Proving equivalence

---

- Again will use an implication table.
  - Only this time, it is the full square.
  - Along bottom are the states of one machine
  - Along the side are the states of the second.
- Start by removing output incompatible states.
 
# The equivalence implication table

- X squares where the outputs are incompatible
- Enter implied equivalence pairs for remaining states.



$S_0$	X	$C-S_3$ $D-S_1$	$A-S_3$ $C-S_1$	X
$S_1$	$B-S_3$ $A-S_0$	X	X	$C-S_3$ $B-S_0$
$S_2$	$B-S_0$ $A-S_2$	X	X	$C-S_0$ $B-S_2$
$S_3$	X	$C-S_2$ $D-S_3$	$A-S_2$ $C-S_3$	X
	A	B	C	D

(a)

# Step 2

- Go back through and remove the implied equivalence pairs that were Xed on the first pass. Continue until no further Xs are entered.
- If there is one square not Xed in each row and each column, the state machines are equivalent. (When both are minimal)
- Consider problem 15-17 in text Does this work if the state tables are of different size?

$s_0$	X	$C-S_3$ $D-S_1$	<del><math>A-S_3</math></del> <del><math>E-S_1</math></del>	X
$s_1$	<del><math>B-S_3</math></del> <del><math>A-S_0</math></del>	X	X	$C-S_3$ $B-S_0$
$s_2$	$B-S_0$ $A-S_2$	X	X	<del><math>C-S_0</math></del> <del><math>B-S_2</math></del>
$s_3$	X	<del><math>C-S_2</math></del> <del><math>D-S_3</math></del>	$A-S_2$ $C-S_3$	X
	A	B	C	D

(b)



# Problem 15.17

## □ The problem statement

15.17 Circuits  $N$  and  $M$  have the state tables that follow.

- Without first reducing the tables, determine whether circuits  $N$  and  $M$  are equivalent.
- Reduce each table to a minimum number of states, and then show that  $N$  is equivalent to  $M$  by inspecting the reduced tables.

$M$				$N$			
	$X = 0$	$1$		$X = 0$	$1$		
$S_0$	$S_3$	$S_1$	$0$	$A$	$E$	$A$	$1$
$S_1$	$S_0$	$S_1$	$0$	$B$	$F$	$B$	$1$
$S_2$	$S_0$	$S_2$	$1$	$C$	$E$	$D$	$0$
$S_3$	$S_0$	$S_3$	$1$	$D$	$E$	$C$	$0$
				$E$	$B$	$D$	$0$
				$F$	$B$	$C$	$0$

# Problem 15.17

---

- Can be Worked on board
- Or here in the slides
  - Start with an equivalence implication table

	A	B	C	D	E	F
S0						
S1						
S2						
S3						

# Output compatible

- Go through and X output incompatible states

	A	B	C	D	E	F
S0	X	X				
S1	X	X				
S2			X	X	X	X
S3			X	X	X	X

# Next State

- Fill in the next state pairs on the table

	A	B	C	D	E	F
S0	X	X	S3 - E S1 - D	S3 - E S1 - C	S3 - B S1 - D	S3 - B S1 - C
S1	X	X	S0 - E S1 - D	S0 - E S1 - C	S0 - B S1 - D	S0 - B S1 - C
S2	S0 - E S2 - A	S0 - F S2 - B	X	X	X	X
S3	S0 - E S3 - A	S0 - F S3 - B	X	X	X	X


# 1<sup>st</sup> Pass through table

- Check implied pairs (S3-E)x (S0-B)x
  - Remainder are compatible. It seems machine has redundant states

	A	B	C	D	E	F
S0	X	X	S3 - E S1 - D	S3 - E S1 - C	S3 - B S1 - D	S3 - B S1 - C
S1	X	X	S0 - E S1 - D	S0 - E S1 - C	S0 - B S1 - D	S0 - B S1 - C
S2	S0 - E S2 - A	S0 - F S2 - B	X	X	X	X
S3	S0 - E S3 - A	S0 - F S3 - B	X	X	X	X
 
# Minimize both machines?

- Start with the  $S_x$  machine – can it be minimized? If so, what are implications?





15.17 Circuits  $N$  and  $M$  have the state tables that follow.

- Without first reducing the tables, determine whether circuits  $N$  and  $M$  are equivalent.
- Reduce each table to a minimum number of states, and then show that  $N$  is equivalent to  $M$  by inspecting the reduced tables.

$M$				$N$			
	$X=0$	$1$		$X=0$	$1$		
$S_0$	$S_3$	$S_1$	0	$A$	$E$	$A$	1
$S_1$	$S_0$	$S_1$	0	$B$	$F$	$B$	1
$S_2$	$S_0$	$S_2$	1	$C$	$E$	$D$	0
$S_3$	$S_0$	$S_3$	1	$D$	$E$	$C$	0
				$E$	$B$	$D$	0
				$F$	$B$	$C$	0

# Minimize both machines

## □ Implied Next States

 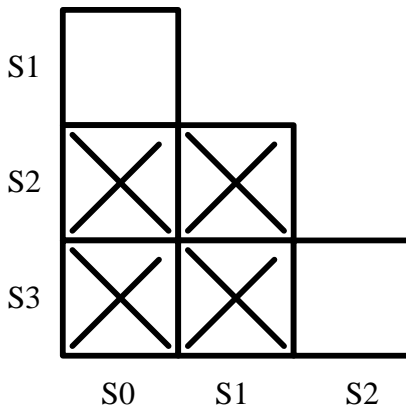




15.17 Circuits  $N$  and  $M$  have the state tables that follow.

- Without first reducing the tables, determine whether circuits  $N$  and  $M$  are equivalent.
- Reduce each table to a minimum number of states, and then show that  $N$  is equivalent to  $M$  by inspecting the reduced tables.

$M$				$N$			
	$X=0$	$1$		$X=0$	$1$		
$S_0$	$S_3$	$S_1$	$0$	$A$	$E$	$A$	$1$
$S_1$	$S_0$	$S_1$	$0$	$B$	$F$	$B$	$1$
$S_2$	$S_0$	$S_2$	$1$	$C$	$E$	$D$	$0$
$S_3$	$S_0$	$S_3$	$1$	$D$	$E$	$C$	$0$
				$E$	$B$	$D$	$0$
				$F$	$B$	$C$	$0$

# Minimize both machines


□ Can it be reduced?

   


 
# Reduced machine

- Can be seen from state graph
- States S2 and S3 are equivalent – in fact S2 is not reachable unless the machine comes up in that state at startup and it can never reach S2 again.




# Now for the A,B,...,E machine

## □ Start with incompatible outputs

15.17 Circuits  $N$  and  $M$  have the state tables that follow.



- (a) Without first reducing the tables, determine whether circuits  $N$  and  $M$  are equivalent.  
 (b) Reduce each table to a minimum number of states, and then show that  $N$  is equivalent to  $M$  by inspecting the reduced tables.

$M$				$N$			
	$X=0$	$1$		$X=0$	$1$		
$S_0$	$S_3$	$S_1$	0	$A$	$E$	$A$	1
$S_1$	$S_0$	$S_1$	0	$B$	$F$	$B$	1
$S_2$	$S_0$	$S_2$	1	$C$	$E$	$D$	0
$S_3$	$S_0$	$S_3$	1	$D$	$E$	$C$	0
				$E$	$B$	$D$	0
				$F$	$B$	$C$	0

 

# And then implied next state

- And run through algorithm

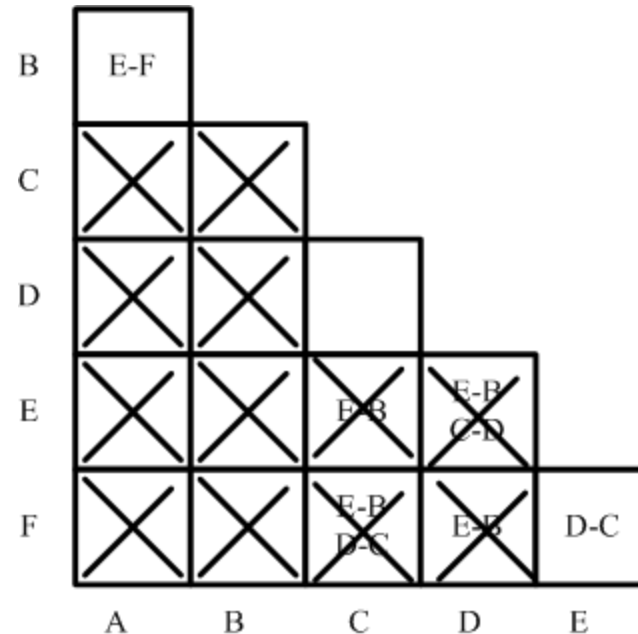 

# Result is reduced state table

## □ Find that

- $D \equiv C$
- $E \equiv F$
- $A \equiv B$

## □ So state table reduces to AND for $S_x$ version

	X=0	X=1	OUTPUT
A	E	A	1
C	E	C	0
E	A	C	0

	X=0	X=1	OUTPUT
S3	S0	S3	1
S1	S0	S1	0
S0	S3	S1	0

# Significance

- Now consider the equivalence implication table. What is the implication if S2 replaces state S2 and S3?

	A	B	C	D	E	F
S0	X	X	<del>S3 - E S1 - D</del>	<del>S3 - E S1 - C</del>	S3 - B S1 - D	S3 - B S1 - C
S1	X	X	S0 - E S1 - D	S0 - E S1 - C	<del>S0 - B S1 - D</del>	<del>S0 - B S1 - C</del>
S2	S0 - E S2 - A	S0 - F S2 - B	X	X	X	X
S3	S0 - E S3 - A	S0 - F S3 - B	X	X	X	X



# Incompletely Specified

---

- Incompletely Specified State Tables
  - State tables that contain don't cares.
  - Results in reduced logic
  
- Determining the best way to fill in the don't cares is another of the *n-p complete* problems.
- For this course do the most logical approach.



# One Hot

---

- CPLDs and FPGAs have a good number of F/Fs onboard. The F/Fs are there whether they are used or not, so a circuit with the minimum number of F/Fs is not the ultimate objective.
- For these devices the objective is to reduce the total number of logic cells used and the interconnection between cells.
- One hot encoding is one approach to have shorter signal paths and reduce logic cells.



# What is one hot?


---

- ❑ One hot is a method where a flip flop is used for each state in the state machine. A state machine with  $n$  states will require  $n$  flip flops in its realization.
- ❑ One hot realization is excellent for controllers that step through a set sequence of linear steps.
- ❑ Text gives example of a multiplier controller state graph which is not linear.


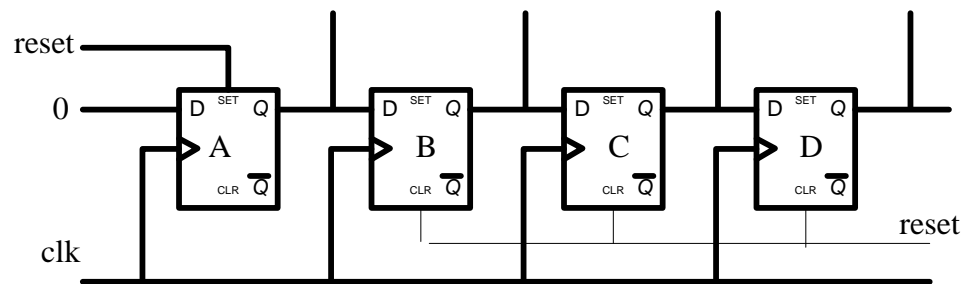
# Linear one hot

- Linear one hot sequential controllers requires no next state logic.
- On Reset the output of the 4 F/F is 1000
  - On clocks 0100, then 0010, then 0001, then 0000






# One hot use

---

- Have been use in such things as
  - Successive approximation A-D converters
  - Various automotive control systems
  - Automated machinery control systems
- Also commonly used in processor controllers
  - Process controller states
    - F1,F2,F3,F4,F5,F6,F7,F8 always followed by
    - E0,E1,E2,E3,E4,E5,E6,E7 if direct addressing
    - E20,E21,E22,E23,E24,E25,E26,E27 if indirect

 
# One hot application

- One hot could have been used in the sequence detector problems
  - Detect an input sequence ending in 101.
  - Construct a shift register that holds the last 3 inputs of an input  $X$ .


 
# The full circuit

- Desire  $Z=1$  when  $X_{-1} X_{-2} X_{-3}$  is 101.
- Simply construct the combinational logic with inputs from the F/F outputs.






# Compare the gates

---

- Traditional implementation for sequence detector (from text)
  - 2 F/Fs
  - 2 2-input AND gates
  - 1 INV
  
- One hot implementation
  - 3 F/Fs
  - 1 3-input AND gate

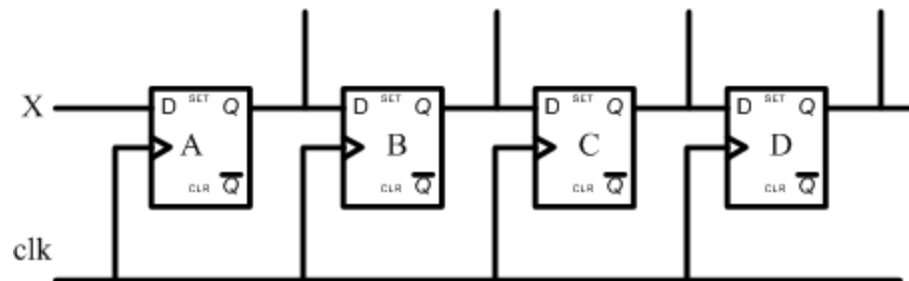
# Another example

- Design a sequence detector that detects input sequences ending in 010 or 1001.  $Z = 1$  when a sequence is detected.
- Start with a 4 bit shift register to hold the last 4 inputs.


 
# Now add Z generation logic

- Construct the combinational logic for Z




# Implementation comparison

## □ Traditional

- 3 F/Fs
- Need to work problem
- more than 1 hot
 
## □ One hot


- 4 F/Fs
- 2 AND gates (1- 3 inp, 1- 4 inp)
- 1 OR gate (2 inp)





# The state table

□ For the Mealy Machine

 

Present State	NEXT STATE		OUTPUT	
	X=0	X=1	X=0	X=1
S0	S1	S4	0	0
S1	S1	S2	0	0
S2	S3	S4	1	0
S3	S5	S2	0	0
S4	S3	S4	0	0
S5	S1	S2	0	1

# Comparison

---

- This was worked to gates in lect 9.
  - 3 D F/Fs
  - 2 – 3 input AND gates
  - 3 – 2 input AND gates
  - 2 – 2 input OR gates
  - 1 – 3 input OR gate
- Versus one hot
  - 4 F/Fs
  - 1 – 3 input AND gate
  - 1 – 4 input AND gate
  - 1 – 2 input OR
- Comments from class??????



# Lecture summary

---

- Have looked at state machine equivalence.
- Incompletely specified machine implication.
- One hot encoding and how it may not be all that bad an alternative.